

# Gajendra Processor

Lab Report

submitted by

P . Yashwanth Sai (CS22B002), V . Yaswanth Sai (CS22B043)

Under the supervision

of

Dr.Ayon Chakraborty



Computer Science and Engineering

Indian Institute of Technology Madras

Jul - Nov 2023

# Contents

|          |                                       |           |
|----------|---------------------------------------|-----------|
| <b>1</b> | <b>General CPU Register</b>           | <b>5</b>  |
| 1.1      | Diagram . . . . .                     | 5         |
| 1.2      | I/O Control . . . . .                 | 5         |
| 1.3      | Working . . . . .                     | 5         |
| <b>2</b> | <b>Program Counter</b>                | <b>5</b>  |
| 2.1      | Diagram . . . . .                     | 5         |
| 2.2      | PC_INC . . . . .                      | 6         |
| 2.3      | PC_OUT . . . . .                      | 6         |
| 2.4      | PC_LOAD . . . . .                     | 6         |
| <b>3</b> | <b>MEMORY</b>                         | <b>7</b>  |
| 3.1      | Diagram . . . . .                     | 7         |
| 3.2      | Diagram . . . . .                     | 7         |
| 3.3      | MEM_OUT . . . . .                     | 7         |
| <b>4</b> | <b>MEMORY ADDRESS REGISTER</b>        | <b>7</b>  |
| 4.1      | MAR_IN . . . . .                      | 8         |
| <b>5</b> | <b>INSTRUCTION REGISTER</b>           | <b>8</b>  |
| 5.1      | Diagram . . . . .                     | 8         |
| 5.2      | INS_REG_IN . . . . .                  | 8         |
| 5.3      | INS_REG_OUT . . . . .                 | 8         |
| 5.4      | CTRL . . . . .                        | 9         |
| <b>6</b> | <b>INSTRUCTION DECODER</b>            | <b>9</b>  |
| 6.1      | Diagram . . . . .                     | 9         |
| 6.2      | INS_DEC_OUT . . . . .                 | 9         |
| 6.3      | ALU_OUT . . . . .                     | 9         |
| <b>7</b> | <b>Arithmetic and Logic Unit(ALU)</b> | <b>10</b> |
| 7.1      | ADD . . . . .                         | 10        |
| 7.2      | SUB . . . . .                         | 10        |
| 7.3      | SHIFT . . . . .                       | 10        |
| <b>8</b> | <b>Status Register</b>                | <b>11</b> |
| 8.1      | Diagram . . . . .                     | 11        |
| 8.2      | I/O . . . . .                         | 11        |
| 8.3      | Uses . . . . .                        | 11        |
| <b>9</b> | <b>Control Processor</b>              | <b>12</b> |
| 9.1      | Diagram . . . . .                     | 12        |
| 9.2      | I/O . . . . .                         | 12        |
| 9.3      | Working . . . . .                     | 12        |
| 9.4      | Ring Counter . . . . .                | 12        |
| 9.5      | EEPROM Programming . . . . .          | 13        |

|   |           |
|---|-----------|
| <b>10 Microinstructions and Controller Logic Design</b> | <b>13</b> |
| 10.1 NOP :  | 13        |
| 10.2 LDA :  | 13        |
| 10.3 ADD :  | 13        |
| 10.4 SUB :  | 14        |
| 10.5 LDI :  | 14        |
| 10.6 JMP :  | 14        |
| 10.7 SWAP :   | 15        |
| 10.8 JNZ :  | 15        |
| 10.9 MOVAB :  | 15        |
| 10.10MOVBA :  | 16        |
| 10.11LSHIFT :   | 16        |
| 10.12RSHIFT :   | 16        |
| 10.13OUT :  | 16        |
| 10.14HLT :  | 17        |
| <b>11 Instruction Set</b>                               | <b>18</b> |
| 11.1 NOP :  | 18        |
| 11.2 LDA :  | 18        |
| 11.3 ADD :  | 18        |
| 11.4 SUB :  | 19        |
| 11.5 LDI :  | 20        |
| 11.6 JMP :  | 20        |
| 11.7 SWAP :   | 21        |
| 11.8 JNZ :  | 21        |
| 11.9 MOVAB :  | 21        |
| 11.10MOVBA :  | 22        |
| 11.11LSHIFT :   | 23        |
| 11.12RSHIFT :   | 23        |
| 11.13OUT :  | 23        |
| 11.14HLT :  | 24        |
| <b>12 Sample programs</b>                               | <b>25</b> |
| 12.1 For Addition and Subtraction                       | 25        |
| 12.2 For L-shift  | 25        |
| 12.3 For Multiplication                                 | 25        |

## List of Figures

|    |  |    |
|----|--|----|
| 1  | 8-bit Register . . . . .               | 5  |
| 2  | Program Counter . . . . .              | 6  |
| 3  | Memory . . . . .                       | 7  |
| 4  | EEPROM . . . . .                       | 7  |
| 5  | Instruction Register . . . . .         | 8  |
| 6  | Instruction Decoder . . . . .          | 9  |
| 7  | Gajendra ALU . . . . .                 | 10 |
| 8  | Status Register . . . . .              | 11 |
| 9  | Control Processor . . . . .            | 12 |
| 10 | Micro Instruction for NOP . . . . .    | 13 |
| 11 | Micro instruction for LDA . . . . .    | 13 |
| 12 | Micro instruction for ADD . . . . .    | 13 |
| 13 | Micro instruction for SUB . . . . .    | 14 |
| 14 | Micro instruction for LDI . . . . .    | 14 |
| 15 | Micro instruction for JMP . . . . .    | 14 |
| 16 | Micro instruction for SWAP . . . . .   | 15 |
| 17 | Micro instruction for JNZ . . . . .    | 15 |
| 18 | Micro instruction for MOVAB . . . . .  | 15 |
| 19 | Micro instruction for MOVBA . . . . .  | 16 |
| 20 | Micro instruction for LSHIFT . . . . . | 16 |
| 21 | Micro instruction for RSHIFT . . . . . | 16 |
| 22 | Micro instruction for OUT . . . . .    | 17 |
| 23 | Micro instruction for HLT . . . . .    | 17 |
| 24 | Instruction Set for NOP . . . . .      | 18 |
| 25 | Instruction Set for LDA . . . . .      | 18 |
| 26 | Instruction Set for ADD . . . . .      | 19 |
| 27 | Instruction Set for SUB . . . . .      | 19 |
| 28 | Instruction Set for LDI . . . . .      | 20 |
| 29 | Instruction Set for JMP . . . . .      | 20 |
| 30 | Instruction for SWAP . . . . .         | 21 |
| 31 | Instruction Set for JNZ . . . . .      | 21 |
| 32 | Instruction Set for MOVAB . . . . .    | 22 |
| 33 | Instruction Set for MOVBA . . . . .    | 22 |
| 34 | Instruction Set for LSHIFT . . . . .   | 23 |
| 35 | Instruction Set for RSHIFT . . . . .   | 23 |
| 36 | Instruction Set for OUT . . . . .      | 24 |
| 37 | Instruction Set for HLT . . . . .      | 24 |

# 1 General CPU Register

## 1.1 Diagram

 


Figure 1: 8-bit Register

## 1.2 I/O Control

It takes 8-bit input from the common bus. Which is stored in it. The 8-bit value stored in it is given as output. REG\_in and REGout are used as the control inputs for controlling the input and output.

## 1.3 Working

If REG\_in is 1 the input is read from the common bus and when REG\_out is 1 the output is written to the common bus.

# 2 Program Counter

## 2.1 Diagram

The ROM consists of both the instructions and data for the program that has to be run , The program counter points to the address of the instruction in ROM , that has to be processed

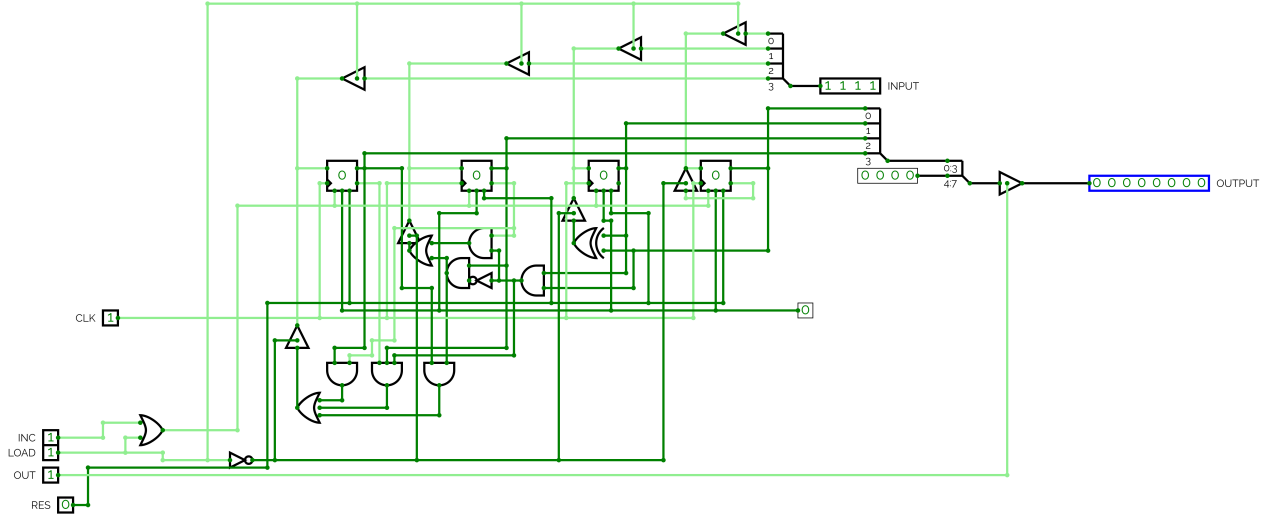


Figure 2: Program Counter

next . At the starting of the program the program counter is reset to 0000 , It then sends the address that is stored in it (i.e 0000 in this case) to the Memory Address Register , The program counter is then incremented by 1 (i.e to 0001 in this case) , After the first instruction is executed then the program counter sends the current address stored in it (i.e 0001 in this case) , this cycle keeps on repeating until the program ends.

The following are the functionalities that are present in the Program Counter.

## 2.2 PC\_INC

If  $PC\_INC = 1$  then the value of the address stored in the Program Counter is incremented by 1 in each positive clock triggering .

## 2.3 PC\_OUT

If  $PC\_OUT = 1$  then the Program Counter sends the address stored in it into the Least Significant Bits (0-3) of the **common bus** of the **Gajendra Processor** through **output** .

## 2.4 PC\_LOAD

If  $PC\_LOAD = 1$  then the Program Counter takes the Least Significant Bits (0-3) of the **common bus** into it through the **input** and stores it as the next instruction .

## 3 MEMORY

### 3.1 Diagram

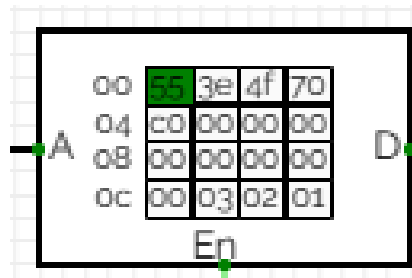


Figure 3: Memory

### 3.2 Diagram

 


Figure 4: EEPROM

Memory is a ROM which contains both instruction and data required for a program. The following are the functionalities that are present in the Memory. We are using EEPROM here for STA instruction .

### 3.3 MEM\_OUT

If  $\text{MEM\_OUT} = 1$  then the memory releases a 8-bit output into the common bus.

## 4 MEMORY ADDRESS REGISTER

During a computer run , the 4-bit address in the Programming Counter is latched into the MAR .Then the MAR applies this 4-bit address to the Memory where a read operation is performed. The following are the functionalities that are present in the MAR .

## 4.1 MAR\_IN

If  $MAR\_IN = 1$  , then the MAR takes the 4-bit address (Least Significant in common bus) from the Program Counter through common bus.

# 5 INSTRUCTION REGISTER

## 5.1 Diagram

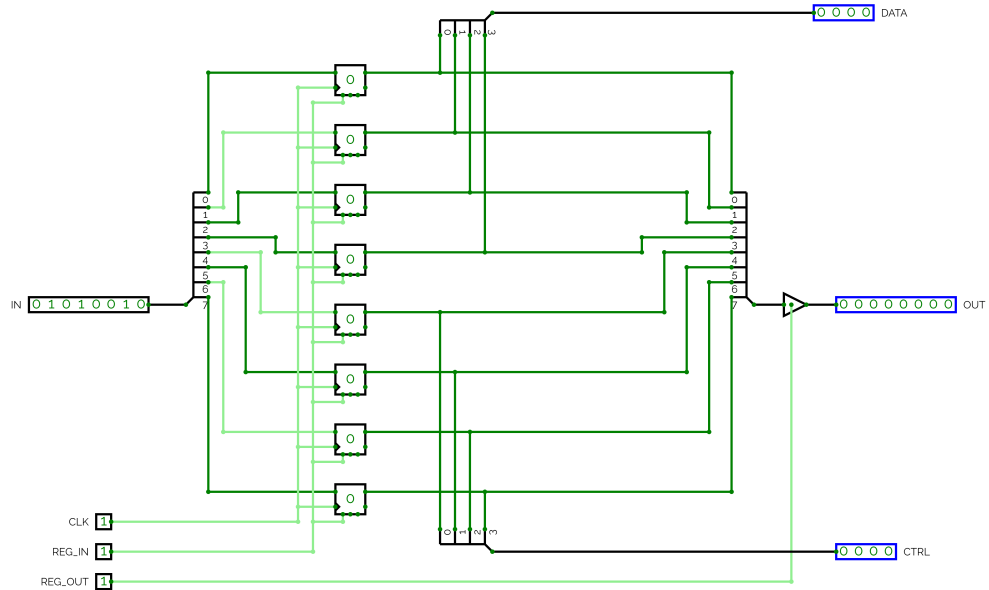


Figure 5: Instruction Register

To fetch an instruction from the memory the computer does a memory read operation . This places the contents of the addressed memory location on the common bus. The instruction register loads this content into it on the next positive clock edge .

The contents of the instruction register are split into two nibbles of 4-bits each (least 4 significant bits , most 4-significant bits) , The most 4-significant bits are sent into **Controller** and it will also send the 8-bit content into the **Instruction decoder** .

The following are the functionalities that are present in the Instruction register .

## 5.2 INS\_REG\_IN

If  $INS\_REG\_IN = 1$  , then the INS register takes the 8-bit content as input from the common bus .

## 5.3 INS\_REG\_OUT

If  $INS\_REG\_OUT = 1$  , then INS register loads its 8-bit content into Instruction decoder which further enter into the common bus .



## 5.4 CTRL

The Most Significant 4-bits(4-7) automatically goes to the **Controller** and **INS Decoder** as instruction from INS Register.

# 6 INSTRUCTION DECODER

## 6.1 Diagram

 


Figure 6: Instruction Decoder

It helps the ALU by giving the instruction whether to add or subtract , by using the most significant 4-bits (i.e CTRL) . It also helps us with the instruction **LDI** by making the 4 - most significant bits into 0000 , so that the remaining 4-bits gets stored in our **accumulator (i.e register A)**.

The following are the functionalities that are present in the Instruction Decoder .

## 6.2 INS \_DEC \_OUT

If  $INS\_DEC\_OUT = 1$  , then it takes the 8-bit content from OUT of INS register .

## 6.3 ALU\_OUT

The INS\_DEC generates a 2-bit input for the **ALU**.

It generates the following outputs for the corresponding instructions .

00  $\implies$  *Addition*

01  $\implies$  *Subtraction*

10  $\implies$  *LShift*

11  $\implies$  *RShift*

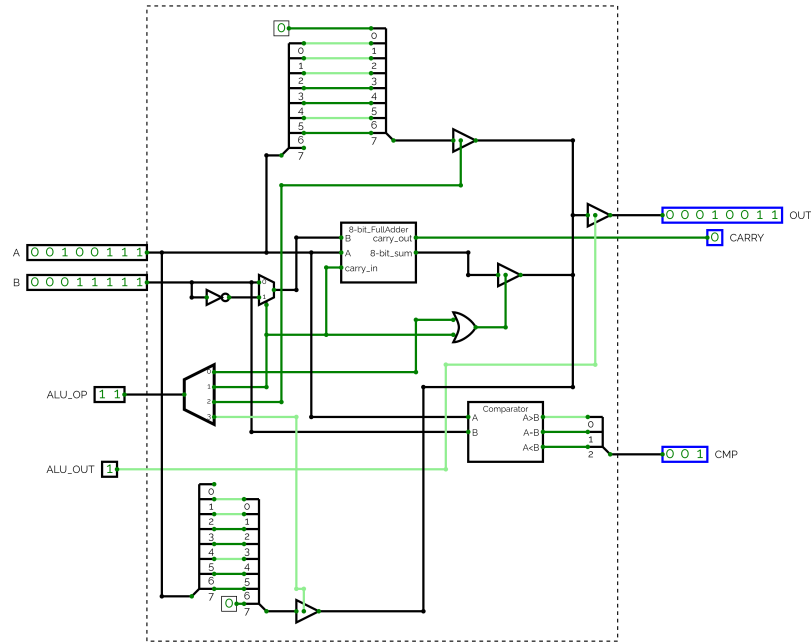


Figure 7: Gajendra ALU

## 7 Arithmetic and Logic Unit(ALU)

The ALU performs the arithmetic operations that are executed by the computer. The operations that are supported are Addition(ADD) , Subtraction(SUB) and SHIFT . It stores the final value in it and it also returns the final 8-bit into Accumulator or REG \_A .

### 7.1 ADD

The ADD operation is used to add two 8-bit numbers using a 8-bit full adder which adds without carry .

### 7.2 SUB

The SUB operation is used to subtract two 8-bit numbers using a 8-bit full adder with an input from the INS\_DEC which triggers sub operation.

### 7.3 SHIFT

The LSHIFT operation performs a bitwise left shift on the value in register A whereas the RSHIFT operation performs a bitwise right shift on the value in register A.

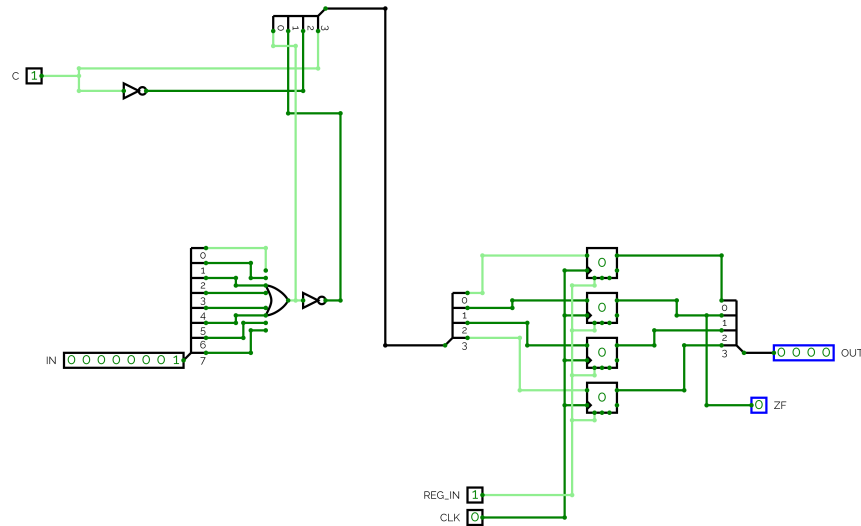


Figure 8: Status Register

## 8 Status Register

### 8.1 Diagram

### 8.2 I/O

It takes 2 inputs ALU \_OUT and Carry from ALU and gives a 4-bit output in which the **the most significant bit is C**(1 if carry = 1) and the next bit gives **NC**( $\overline{C}$ ) and the next bit gives **Z**(1 if(ALU \_OUT = 1) and the least significant gives **NZ**  $\overline{Z}$  .

### 8.3 Uses

It is used to implement JUMP and JUMP if zero conditions .

## 9 Control Processor

### 9.1 Diagram

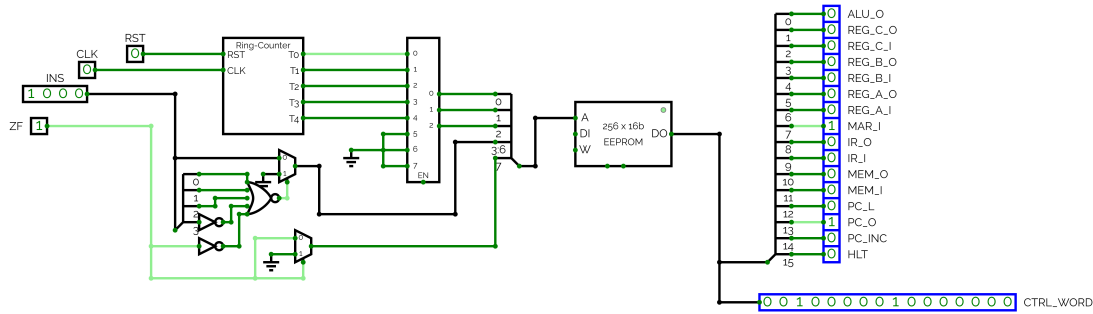


Figure 9: Control Processor

### 9.2 I/O

The control processor takes 4 bit instruction as input and we use a ring counter of length 5 indicating the 5 T-states. The EEPROM in the control processor takes 8-bit address in which the first bit is inherently zero and next 4 bits are the instruction and the last 3 bits are the T-state that is to be implemented. The EEPROM gives 16-bit output which is the control word which is also the output of the Control Processor.

### 9.3 Working

This control word controls all the other elements like REG\_in, REG\_out, PC\_load, PC\_out, PC\_inc, flag, MEM\_in, MEM\_out, MAR\_in, INS\_out, INS\_out, ALU\_out. The control processor is the most important component of our processor as it controls all the other components. When Ins is 1000 (JNZ) and ZF = 1, this instruction changes to NOP (0000) and the MSB of address entering into EEPROM will also be 0 (i.e the ZF will enter A as 0). In this way other half of the EEPROM need not be wasted and optimized.

### 9.4 Ring Counter

Every instruction has some micro instructions called T-states that are to be executed in order one at a time, these control words are generated by accessing the memory locations in the EEPROM, the T-states are governed by the ring counter.

## 9.5 EEPROM Programming

The EEPROM is loaded in such a way that every instruction has 8 memory locations in the EEPROM for its micro instructions. The each memory locations contains the control word of that particular micro instruction.

# 10 Microinstructions and Controller Logic Design

## 10.1 NOP :

|       |                               |    |
|-------|-------------------------------|----|
| NOP : | 1<<PC_OUT 1<<MAR_IN           | T0 |
|       | 1<<PC_INC 1<<MEM_OUT 1<<IR_IN | T1 |
|       | 0                             | T2 |
|       | 0                             | T3 |
|       | 0                             | T4 |

Figure 10: Micro Instruction for NOP

## 10.2 LDA :

|       |                               |    |
|-------|-------------------------------|----|
| LDA : | 1<<PC_OUT 1<<MAR_IN           | T0 |
|       | 1<<PC_INC 1<<MEM_OUT 1<<IR_IN | T1 |
|       | 1<<IR_OUT 1<<MAR_IN           | T2 |
|       | 1<<MEM_OUT 1<<REGA_IN         | T3 |
|       | 0                             | T4 |

Figure 11: Micro instruction for LDA

## 10.3 ADD :

|       |                               |    |
|-------|-------------------------------|----|
| ADD : | 1<<PC_OUT 1<<MAR_IN           | T0 |
|       | 1<<PC_INC 1<<MEM_OUT 1<<IR_IN | T1 |
|       | 1<<IR_OUT 1<<MAR_IN           | T2 |
|       | 1<<MEM_IN 1<<REGA_OUT         | T3 |
|       | 0                             | T4 |

Figure 12: Micro instruction for ADD

#### 10.4 SUB :

|     |                               |    |
|-----|-------------------------------|----|
| SUB | :1<<PC_OUT 1<<MAR_IN          | T0 |
|     | 1<<PC_INC 1<<MEM_OUT 1<<IR_IN | T1 |
|     | 1<<IR_OUT 1<<MAR_IN           | T2 |
|     | 1<<MEM_IN 1<<REGA_OUT         | T3 |
|     | 0                             | T4 |

Figure 13: Micro instruction for SUB

#### 10.5 LDI :

|     |                               |    |
|-----|-------------------------------|----|
| LDI | :1<<PC_OUT 1<<MAR_IN          | T0 |
|     | 1<<PC_INC 1<<MEM_OUT 1<<IR_IN | T1 |
|     | 1<<IR_OUT 1<<REGA_IN          | T2 |
|     | 0                             | T3 |
|     | 0                             | T4 |

Figure 14: Micro instruction for LDI

#### 10.6 JMP :

|     |                               |    |
|-----|-------------------------------|----|
| JMP | :1<<PC_OUT 1<<MAR_IN          | T0 |
|     | 1<<PC_INC 1<<MEM_OUT 1<<IR_IN | T1 |
|     | 1<<IR_OUT 1<<PC_LOAD          | T2 |
|     | 0                             | T3 |
|     | 0                             | T4 |

Figure 15: Micro instruction for JMP

## 10.7 SWAP :

|      |                               |    |
|------|-------------------------------|----|
| SWAP | :1<<PC_OUT 1<<MAR_IN          | T0 |
|      | 1<<PC_INC 1<<MEM_OUT 1<<IR_IN | T1 |
|      | 1<<REGA_OUT 1<<REGB_IN        | T2 |
|      | 1<<REGC_OUT 1<<REGA_IN        | T3 |
|      | 1<<REGB_OUT 1<<REGC_IN        | T4 |

Figure 16: Micro instruction for SWAP

## 10.8 JNZ :

|     |                               |    |
|-----|-------------------------------|----|
| JNZ | :1<<PC_OUT 1<<MAR_IN          | T0 |
|     | 1<<PC_INC 1<<MEM_OUT 1<<IR_IN | T1 |
|     | 1<<IR_OUT 1<<PC_LOAD          | T2 |
|     | 0                             | T3 |
|     | 0                             | T4 |

Figure 17: Micro instruction for JNZ

## 10.9 MOVAB :

|       |                               |    |
|-------|-------------------------------|----|
| MOVAB | :1<<PC_OUT 1<<MAR_IN          | T0 |
|       | 1<<PC_INC 1<<MEM_OUT 1<<IR_IN | T1 |
|       | 1<<REGA_OUT 1<<REGB_IN        | T2 |
|       | 0                             | T3 |
|       | 0                             | T4 |

Figure 18: Micro instruction for MOVAB

### 10.10 MOVBA :

|                               |    |
|-------------------------------|----|
| MOVBA:1<<PC_OUT 1<<MAR_IN     | T0 |
| 1<<PC_INC 1<<MEM_OUT 1<<IR_IN | T1 |
| 1<<REGB_OUT 1<<REGA_IN        | T2 |
| 0                             | T3 |
| 0                             | T4 |

Figure 19: Micro instruction for MOVBA

### 10.11 LSHIFT :

|                               |    |
|-------------------------------|----|
| SHIFT:1<<PC_OUT 1<<MAR_IN     | T0 |
| 1<<PC_INC 1<<MEM_OUT 1<<IR_IN | T1 |
| 1<<ALU_OUT 1<<REGA_IN         | T2 |
| 0                             | T3 |
| 0                             | T4 |

Figure 20: Micro instruction for LSHIFT

### 10.12 RSHIFT :

|                               |    |
|-------------------------------|----|
| SHIFT:1<<PC_OUT 1<<MAR_IN     | T0 |
| 1<<PC_INC 1<<MEM_OUT 1<<IR_IN | T1 |
| 1<<ALU_OUT 1<<REGA_IN         | T2 |
| 0                             | T3 |
| 0                             | T4 |

Figure 21: Micro instruction for RSHIFT

### 10.13 OUT :



|     |                               |    |
|-----|-------------------------------|----|
| OUT | :1<<PC_OUT 1<<MAR_IN          | T0 |
|     | 1<<PC_INC 1<<MEM_OUT 1<<IR_IN | T1 |
|     | 1<<REGA_OUT 1<<REGC_IN        | T2 |
|     | 0                             | T3 |
|     | 0                             | T4 |

Figure 22: Micro instruction for OUT

#### 10.14 HLT :

|     |                               |    |
|-----|-------------------------------|----|
| HLT | :1<<PC_OUT 1<<MAR_IN          | T0 |
|     | 1<<PC_INC 1<<MEM_OUT 1<<IR_IN | T1 |
|     | 1<<HLT                        | T2 |
|     | 0                             | T3 |
|     | 0                             | T4 |

Figure 23: Micro instruction for HLT

## 11 Instruction Set

### 11.1 NOP :

#### Description

Loads the Instruction Register and increments the Program Counter.

Operation:

(i) (i)None

Syntax:

(i) NOP X

Operands:

None

Program Counter:

$PC \leftarrow PC + 1$

8-bit op-code:

|      |      |
|------|------|
| 0000 | XXXX |
|------|------|

Figure 24: Instruction Set for NOP

### 11.2 LDA :

#### Description

Loads the value stored in the address into the accumulator.

Operation:

(i) (i) $R_A \leftarrow *X$

Syntax:

(i) LDA X

Operands:

$0 \leq x \leq 15$

Program Counter:

$PC \leftarrow PC + 1$

8-bit op-code:

|      |      |
|------|------|
| 0001 | XXXX |
|------|------|

Figure 25: Instruction Set for LDA

### 11.3 ADD :

**Description**

Stores the value in the given address in register B and adds that value to the accumulator.

Operation:

- (i)  $R_B \leftarrow *X$   
 (ii)  $R_A \leftarrow R_A + R_B$

Syntax:

- (i) ADD X

Operands:

$$0 \leq x \leq 15$$

Program Counter:

$$PC \leftarrow PC + 1$$

8-bit op-code:

|      |      |
|------|------|
| 0011 | xxxx |
|------|------|

Figure 26: Instruction Set for ADD

## 11.4 SUB :

**Description**

Stores the value in the given address in register B and subtracts it from the value in the accumulator.

Operation:

- (i)  $R_B \leftarrow *X$   
 (ii)  $R_A \leftarrow R_A - R_B$

Syntax:

- (i) SUB X

Operands:

$$0 \leq x \leq 15$$

Program Counter:

$$PC \leftarrow PC + 1$$

8-bit op-code:

|      |      |
|------|------|
| 0100 | xxxx |
|------|------|

Figure 27: Instruction Set for SUB

## 11.5 LDI :

### Description

Loads the given value into the accumulator.

Operation:

(i)  $(i)R_A \leftarrow X$

Syntax:

(i) LDI X

Operands:

$0 \leq x \leq 15$

Program Counter:

$PC \leftarrow PC + 1$

8-bit op-code:

|      |      |
|------|------|
| 0101 | xxxx |
|------|------|

Figure 28: Instruction Set for LDI

## 11.6 JMP :

### Description

Jumps to the given address unconditionally.

Operation:

(i)  $(i)PC \leftarrow k$

Syntax:

(i) JMP k

Operands:

$0 \leq k \leq 15$

Program Counter:

$PC \leftarrow k$

8-bit op-code:

|      |      |
|------|------|
| 0110 | kkkk |
|------|------|

Figure 29: Instruction Set for JMP

## 11.7 SWAP :

### Description

Swaps the values in registers A and C using the register B.

Operation:

- (i)  $R_B \leftarrow R_A$
- (ii)  $R_A \leftarrow R_C$
- (iii)  $R_C \leftarrow R_B$

Syntax:

- (i) SWAP X

Operands:

$$0 \leq x \leq 15$$

Program Counter:

$$PC \leftarrow PC + 1$$

8-bit op-code:

|      |      |
|------|------|
| 0111 | xxxx |
|------|------|

Figure 30: Instruction for SWAP

## 11.8 JNZ :

### Description

Jumps to the given address only if the NZ flag is 0 else it acts as NOP.

Operation:

- (i)  $PC \leftarrow k / PC \leftarrow PC + 1$

Syntax:

- (i) JNZ X

Operands:

$$0 \leq x \leq 15$$

Program Counter:

$$PC \leftarrow k / PC \leftarrow PC + 1$$

8-bit op-code:

|      |      |
|------|------|
| 1000 | xxxx |
|------|------|

Figure 31: Instruction Set for JNZ

## 11.9 MOVAB :

**Description**

Copies the value in register B to register A and retains the value in register B.

Operation:

(i)  $(i)R_A \leftarrow R_B$

Syntax:

(i) MOVAB X

Operands:

$0 \leq x \leq 15$

Program Counter:

$PC \leftarrow PC + 1$

8-bit op-code:

|      |      |
|------|------|
| 1001 | xxxx |
|------|------|

Figure 32: Instruction Set for MOVAB

### 11.10 MOVBA :

**Description**

Copies the value in register B to register A and retains the value in register B.

Operation:

(i)  $(i)R_B \leftarrow R_A$

Syntax:

(i) MOVBA X

Operands:

$0 \leq x \leq 15$

Program Counter:

$PC \leftarrow PC + 1$

8-bit op-code:

|      |      |
|------|------|
| 1010 | xxxx |
|------|------|

Figure 33: Instruction Set for MOVBA

### 11.11 LSHIFT :

### Description

Bitwise shifts the value in register A by one bit to the left, discarding the leftmost bit and introducing a zero at the rightmost bit.

Operation:

(i) (i)  $R_A \ll 1$

Syntax:

(i) LSHIFT X

Operands:

$$0 \leq x \leq 15$$

Program Counter:

$$PC \leftarrow PC + 1$$

8-bit op-code:

|      |      |
|------|------|
| 1011 | XXXX |
|------|------|

Figure 34: Instruction Set for LSHIFT

## 11.12 RSHIFT :

### Description

Bitwise shifts the value in register A by one bit to the right, discarding the rightmost bit and introducing a zero at the leftmost bit.

Operation:

(i) (i)  $R_A \gg 1$

Syntax:

(i) RSHIFT X

Operands:

$$0 \leq x \leq 15$$

Program Counter:

$$PC \leftarrow PC + 1$$

8-bit op-code:

|      |      |
|------|------|
| 1100 | XXXX |
|------|------|

Figure 35: Instruction Set for RSHIFT

### 11.13 OUT :

**Description**

Copies the value in Register A to Register C and the value is displayed on the screen.

Operation:

- (i)  $(i)R_A \leftarrow X$

Syntax:

- (i) OUT X

Operands:

$$0 \leq x \leq 15$$

Program Counter:

$$PC \leftarrow PC + 1$$

8-bit op-code:

|      |      |
|------|------|
| 1101 | xxxx |
|------|------|

Figure 36: Instruction Set for OUT

## 11.14 HLT :

**Description**

Terminates the program i.e, no further instruction is executed unless the system is restarted.

Operation:

- (i)  $(i)R_A \leftarrow X$

Syntax:

- (i) HLT X

Operands:

$$0 \leq x \leq 15$$

Program Counter:

$$PC \leftarrow PC + 1$$

8-bit op-code:

|      |      |
|------|------|
| 1110 | xxxx |
|------|------|

Figure 37: Instruction Set for HLT



